

DC Circuits I

Physics 2415 Lecture 12

Michael Fowler, UVa

Today's Topics

- Mention of AC
- Semiconductors and superconductors
- Battery emf, internal resistance
- Series and parallel resistances
- Kirchhoff's rules

AC and DC

- **Batteries** provide **direct current, DC**: it always flows in the same direction.
- Almost all electric generators produce a voltage of **sine wave** form:

$$V = V_0 \sin 2\pi ft = V_0 \sin \omega t$$

- This drives an **alternating current, AC**,

$$I = \frac{V_0 \sin \omega t}{R} = I_0 \sin \omega t$$

and power

$$P = VI = I^2 R = I_0^2 R \sin^2 \omega t = \left(V_0^2 / R \right) \sin^2 \omega t$$

AC Average Power and rms Values

- The AC power $P = (V_0^2 / R) \sin^2 \omega t$ varies rapidly ($\omega = 2\pi f$, $f = 60$ Hz here), what is significant for most uses is the **average** power.
- The average value of $\sin^2 \omega t$ is $\frac{1}{2}$.
- Define V_{rms} by $V_{\text{rms}} = \sqrt{\overline{V^2}} = V_0 / \sqrt{2}$
- Then the average power $\overline{P} = V_{\text{rms}}^2 / R$

average value of $\sin^2 \omega t$ must equal average value of $\cos^2 \omega t$. and remember $\sin^2 \omega t + \cos^2 \omega t = 1$

The **standard 120V** AC power is $V_{\text{rms}} = 120\text{V}$.

So the **maximum voltage** V_0 on a 120V line is $120 \times \sqrt{2} = 170\text{V}$!

Sometimes DC *is* used for a Single Long Line

- This 3 gigawatt DC line (enough for 2 to 3 million households) transmits hydropower from the Columbia river to Los Angeles.
- At these distances, it gets tricky synchronizing the phase of AC power.



Semiconductors

- In the Bohr model of the hydrogen atom, an electron circles around a proton.
- An **n-type semiconductor** is a dielectric insulator which has been **doped**—atoms having **one more electron** than the insulator atoms are scattered into it.
- The extra electron circles the dopant atom, but is loosely bound because the dielectric shields the electric field—it looks like a big Bohr atom. As the temperature is raised, these electrons break away from their atoms, and become available to conduct electricity.
- **Bottom Line: Conductivity *increases* with temperature.**

Superconductors

- A superconductor has exactly zero resistivity.
- In 1911, mercury was discovered to superconduct ($R = 0$) when cooled below 4K.
- Superconducting magnets are widely used, in MRI machines, etc.
- There are now materials superconducting above the boiling point of liquid nitrogen, making long distance transmission lines feasible.
- Superconductivity is a quantum phenomenon.

Battery emf \mathcal{E}

- At the terminals inside a battery, a precise voltage is generated by the particular chemical energy exchanges taking place (electron capture or donation by molecules at the terminals).
- This voltage is called the electromotive force (even though it's a potential energy, it *does* drive the current around a circuit), and is denoted by emf or \mathcal{E} .

The emf \mathcal{E} and *Internal Resistance*

- This chemically generated voltage \mathcal{E} also has to push the current through the battery itself.
- The battery has an **internal** resistance, usually denoted by r , so for a current I in the circuit, the battery supplies to the outside world a terminal voltage
 - $V = \mathcal{E} - Ir$
- (This is usually a small effect and can be neglected.)


Resistances in Series

- A battery voltage V pumps a steady current I through 3 resistances in series, as shown.
- Think of the battery as a pump, raising the potential of charge, which then drops in the R 's, like a series of waterfalls $a \rightarrow b \rightarrow c \rightarrow d$.
- From Ohm's Law, the potential drops are:

$$V_{ab} = IR_1, \quad V_{bc} = IR_2, \quad V_{cd} = IR_3.$$


- So the total drop $V = V_{ad} = V_{ab} + V_{bc} + V_{cd} = IR_1 + IR_2 + IR_3 = IR$,

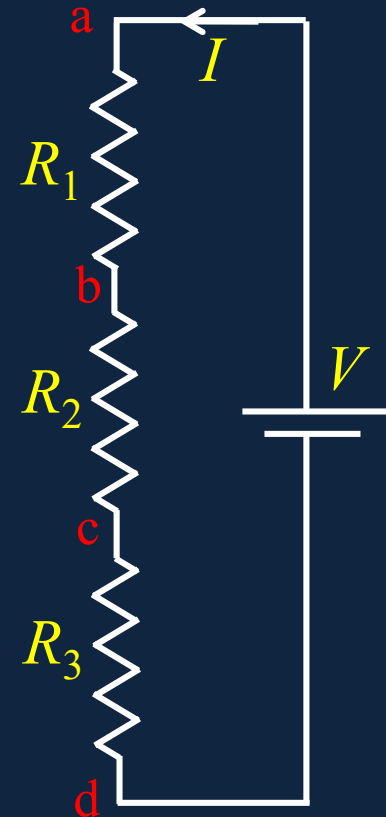where the total resistance $R = R_1 + R_2 + R_3$



Resistances in Parallel

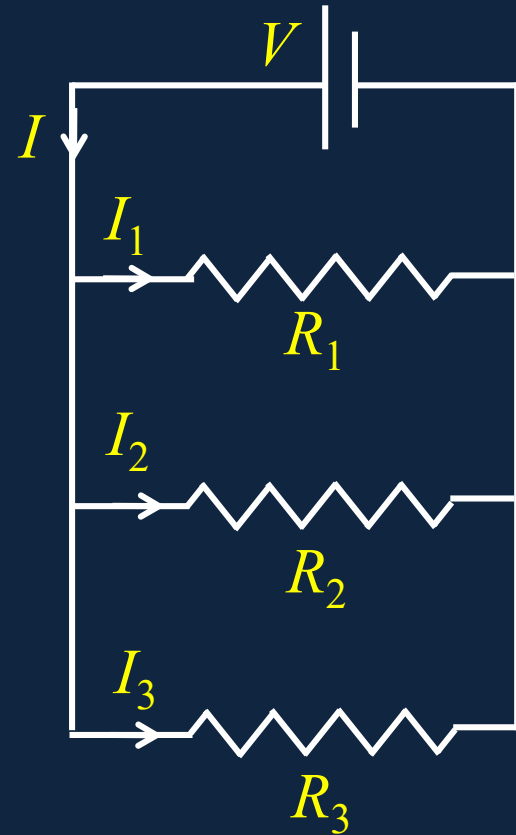- (Convention: lines without zigzag represent wires of negligible resistance.)
- This means **all three** of the resistances shown have the **same voltage V** between their ends.
- So $V = I_1R_1 = I_2R_2 = I_3R_3$
- The total resistance is defined by $V = IR$.
- Now $I = I_1 + I_2 + I_3 = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3} = \frac{V}{R}$,




giving

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

Clicker Question

- Which has the greater **resistance**,
 - A. A 120V 60W bulb?
 - B. A 120V 30W bulb?

Clicker Question


- Which has the greater **resistance**,
 - A. A 120V 60W bulb?
 - B. A 120V 30W bulb? 

Remember power $P = VI = V^2/R$. V is the same for both, so lower R means higher power.

Clicker Question

- If a 60W bulb and a 100W bulb are connected **in series** to a 120V supply, which will be brighter?
 - A. The 60W bulb
 - B. The 100W bulb
 - C. They'll be equally bright

Clicker Answer

- If a 60W bulb and a 100W bulb are connected **in series** to a 120V supply, which will be brighter?
 - A. The 60W bulb 
 - B. The 100W bulb
 - C. They'll be equally bright
 - D. The 60W bulb has greater R , so more voltage drop—and power = VI , they have the same I .


Remember...

- Resistances **in series** all carry the **same current**
- Resistances **in parallel** all have the **same voltage drop**
- Put this together with Ohm's law for each resistance.

General Circuits: Kirchhoff's Rules

- **Junction Rule:** when several wires meet at a point, the total current flowing into the point must equal the total current flowing out. Charge cannot disappear, or pile up at a point.
- **Loop Rule:** the total potential (voltage) change on following wires around a loop to your starting point must be zero.
- *(The loop rule is equivalent to saying that if you follow some random path on a hillside, and get back eventually to your starting point, your net change in height above sea level is zero.)*

Clicker Question

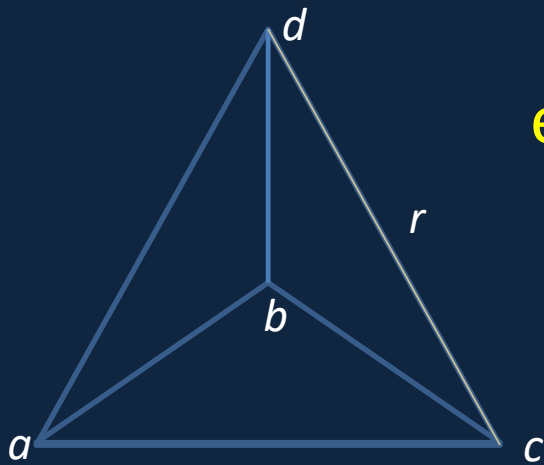


All lines have resistance 1 except dc , which has resistance r .

If a voltage v is applied from a to b , which way does current flow in dc ?

- A. From d to c
- B. From c to d
- C. There is no current

Clicker Answer

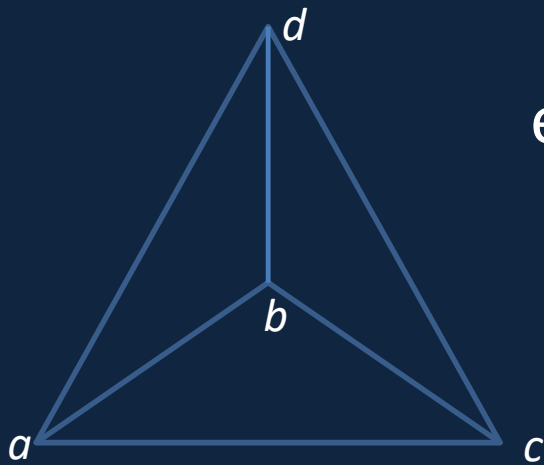


All lines have resistance 1 except dc , which has resistance r .
If a voltage v is applied from a to b , which way does current flow in dc ?

- A. From d to c
- B. From c to d
- C. There is no current

There is **no current** because the situation is **completely symmetrical**: symmetry can sometimes simplify circuit analysis.



Problem

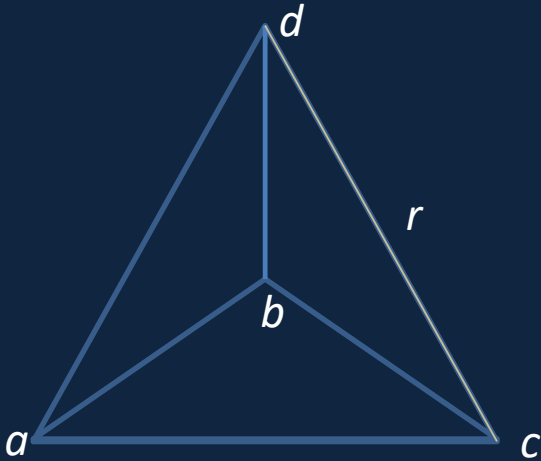

All lines have resistance 1 except dc , which has resistance r .

If now a voltage 10V is applied from a to c , what is the total current flow?